

Vid-01:

Bangladesh Bank

Multimeter: \rightarrow Capable of measuring all important parameter (current, voltage, resistance).

\rightarrow Red probe changed

\rightarrow Voltage and resistance are in same socket.

Voltage measure:

red probe \rightarrow Positive side

black \rightarrow neg side.

Vid-2: Dimming all kinds of LEDs!

PWM \rightarrow Pulse Width Modulation.

Analog tright-function can generate.

square signals. Voltage between 0V to 255V

use potentiometer.

PWM pin 3-

Vid-3: Programming an Arduino

Home made Arduino; shields

Uploadable \rightarrow Attiny-85 \rightarrow also efficient.

8 Kbytes flash memory -

Pin 4 \rightarrow ground

Pin 8 \rightarrow VCC

Pin 5 \rightarrow I/Os

Pin 2, 3, 5, 6, 7 \rightarrow I/O

numbering

0 and 1 PWM signal

Vid-4! Arduino + Bluetooth

Bangladesh Bank


have to use voltage divider to convert 5 volt to 3.3 volt.

two resistors.

52 Terminal App.

RGB LED = 1 anode, 3 cathodes.

TX → Transmit Pin,
RX → Receive Pin

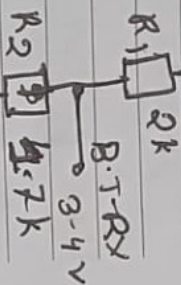

Vid-5: How to Multiplex:

5 anode rows right 10 Cathode Columns down.

→ Controlling Multiple LEDs, individually.

→ Arduino UNO.

→ Fewer pins required, efficient control on multiple displays, ideal for clocks, Timers and counters.

Vid-6! Standalone Arduino

Bangladesh Bank

→ Test your circuit on a breadboard.

4 component:

→ One 16 Mega hertz clock crystal and


→ two 22 PicoFarad capacitors to generate the external clock signal

→ One 10 K Ω resistor connects between ATmega and 5V (VCC)

4 3 ways to change the code.

Kind of old-school are not often used in modern consumer electronics but they are very useful in building small system only outputs a couple numbers on letters-like clock, temperature sensor on the voltage and the current of a power supply.

Use 2.1 volt -

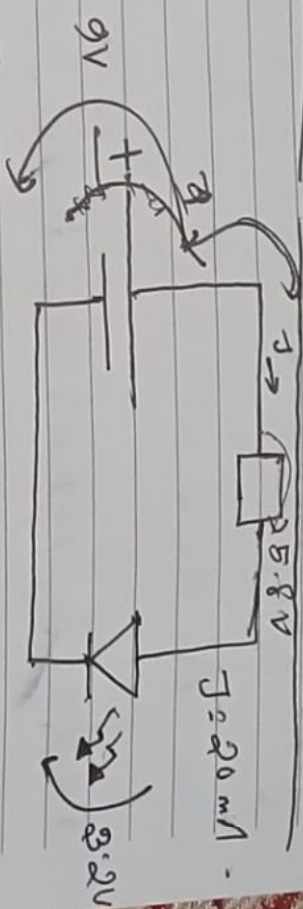

$$\sum V_r = 0$$

$$5.1V = 3.2V + I R \quad R = \frac{V}{I}$$

$$I_R = 5.8V$$

The best way to use LED is not in a constant voltage mode but a constant current mode.

Vid-09: Diode & Bridge Rectifier

diode prevents the circuit from being destroyed in any inrush current is inductive, no diode is perfect.

generate wasted power.

AC \rightarrow DC.

$$P = \frac{1}{T} \int_0^T i^2 R dt \rightarrow \bar{i}^2 R = \frac{1}{T} \int_0^T i^2 R dt$$

$$\bar{i} = \sqrt{\frac{1}{T} \int_0^T i^2 dt} \Rightarrow \bar{i} = i \sin(\omega t)$$

$$\bar{i} = \frac{i}{\sqrt{2}}$$

Bridge Rectifier:

convert neg sin wave to positive

sin wave.

more useful.

Vid-10: Digital to Analog Converter:

Components: Arduino Uno.

- R-2R Resistor Ladder.
- Operational Amplifier (Op-Amp)
- Power supply.

• Used in Audio Generation, signal processing, educational purposes.

This project offers a practical introduction to DACs, showcasing how digital values can be transformed into analog signals using basic components.

Vid 11: Sending SMS with Arduino.

Bangladesh Bank

Max - 6 volts.

3.3v.

Left \rightarrow Ground

Right \rightarrow Module (input).

TX \rightarrow TXDD

RX \rightarrow RXDD

Vid 12: Coils / Induction: (P-1)

more current, more EMF

Induce a voltage, if a conduction moves inside the magnetic field.

MP of plain wire is weak.

Lenz Law: a current will always oppose the change it produces.

Vid 13: Coils / Induction (P-2)

Reactance Bangladesh Bank

Power Oscillates between voltage source and load which obtain



For example: power grid, who know as reactive power.

$$J = \frac{V}{X_L}$$

bigger frequency, more reactance

vid-14)

Bangladesh Bank

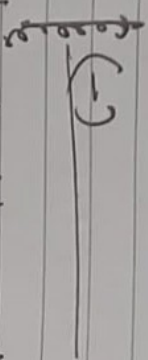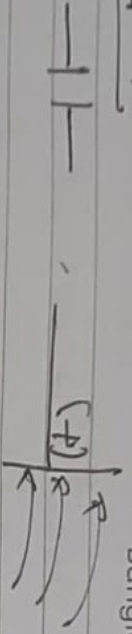

Dielectric material like water increases capacitance.

Electrolytic Capacitor \rightarrow metal sheet with dielectric

Reversing Polarity destroys.

* Basic capacitor \rightarrow metal sheet with dielectric substance in the middle.

* Increasing capacitance \rightarrow bringing the plates closer, using dielectric.

* Switching operation \rightarrow Create diff

signals using resistor creates capacitive reactance X_C in AC

$$X_C \sim \frac{1}{fC}$$


$$X_C = \frac{1}{2\pi fC}, \text{ creates phase shift.}$$

vid-15: Temperature Measurement

Bangladesh Bank

* NTC = Negative Temperature Coefficient Thermistor

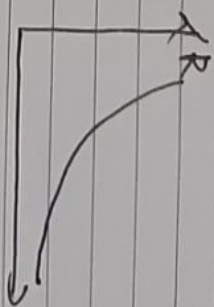* Resistor \rightarrow decrease value as temp. rises.



* PT - 100, 0°C \rightarrow 100 Ω .

Resistance increases with higher Temp max \rightarrow 800°C. * Voltage offset

* Wheatstone Bridge \rightarrow Temp calculating via the change resistance

* 10-turn potentiometer / pre-made transmitter.

* Voltage drop \rightarrow analog input.


* LCD Connect \rightarrow show temp

* LM 35 \rightarrow IC (0-1.5V, 0°-150°C thermal inertia).

vid - 17: Oscillators: RC, LC, Crystal.

using 2 capacitors, alternating 2 resistors.
2 logic AND, 2 logic OR.

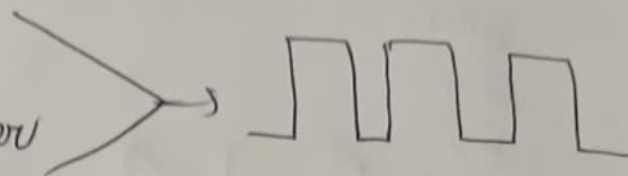→ 100 nF capacitor.
680 Ω res.
150 k Ω potentiometer





$$|X_C| = |X_L|$$

$$\frac{1}{\omega C} = \omega L$$

$$\frac{1}{LC} = \omega^2$$

$$\frac{1}{\sqrt{LC}} = \omega$$

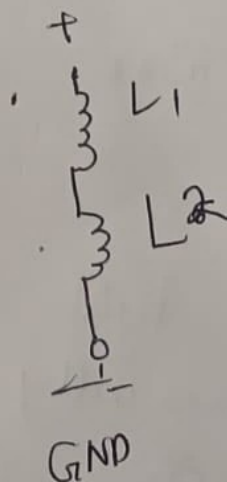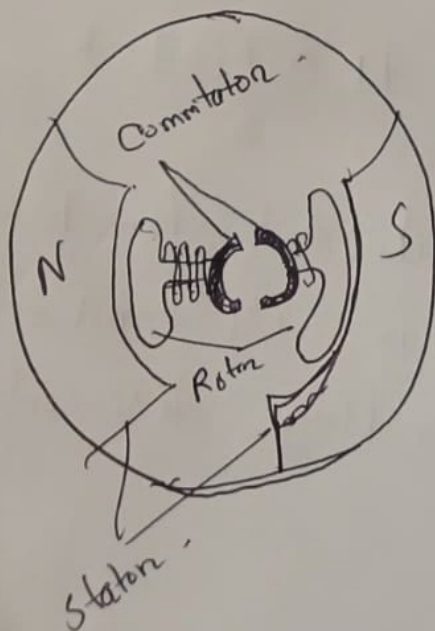vid - 18: Electronic Basics (DC & Brushless DC motor + ESC).



vid-19 I2C and ~~uses~~ its using:

voltage:

GND

(0V)

5V

Binary state (0/1)

0

1

→ Need 2 steps of voltage states to define two binary states of



SCL

SDA





vid 20 Thyristor, Triac, Phase Angle Control,

Diode

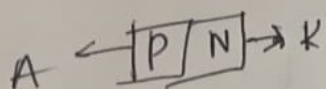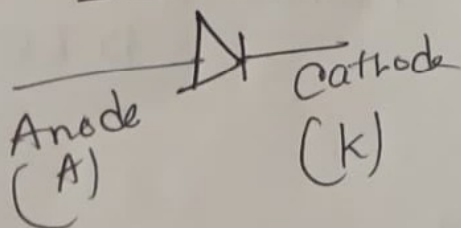

Thyristor

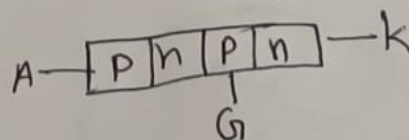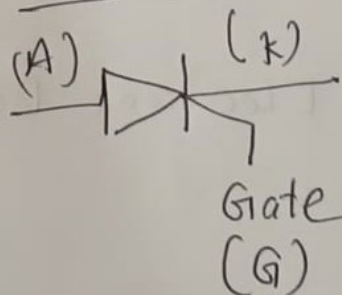

LED does light up but not for long,
Thy is usually stays in its conductive
state even when voltage disconnects

vid 21: OpAmp (Operational Amplifier)

The first golden rule of opamps, ~~gives~~
the output of the opamp will always
attempt everything to keep the voltage
difference between the input at zero volts
 $\Rightarrow +$ and $-$ volts are needed.


$$R_1 = R_2.$$


Rule #3:

vid -22: Transistor (BJT) as a Switch

connect
emitter \rightarrow GND
load between

the supply 3.1V and
supply $V < \text{max collector } V.$

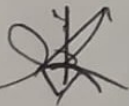~~supply~~ 

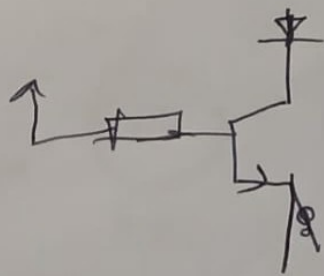

ved-231 Transistor (MOSFET as Switch)


increase efficiency to 97%

MOSFET $\begin{cases} \rightarrow n\text{-channel} \rightarrow \text{Common} \\ \rightarrow p\text{-channel} \end{cases}$

drain \rightarrow drain

anode \rightarrow supply voltage

GND \rightarrow gate

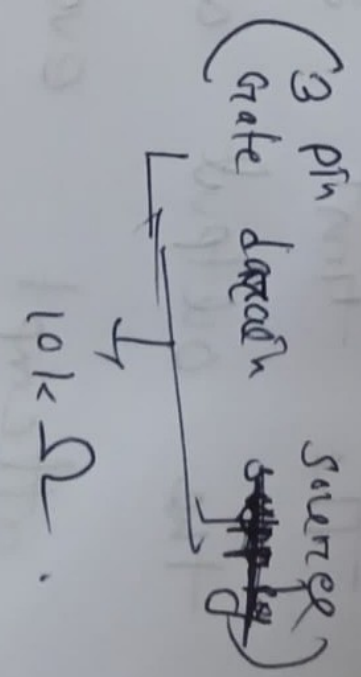

ved 24) Stepper Motors and the uses?

Vid 24:

Codes:

Steps / rotations.

Full $\rightarrow 200$


half $\rightarrow 400$

$1/4 \rightarrow 800$


$1/8 \rightarrow 1600$

$1/16 \rightarrow 3200$

micro
stepping

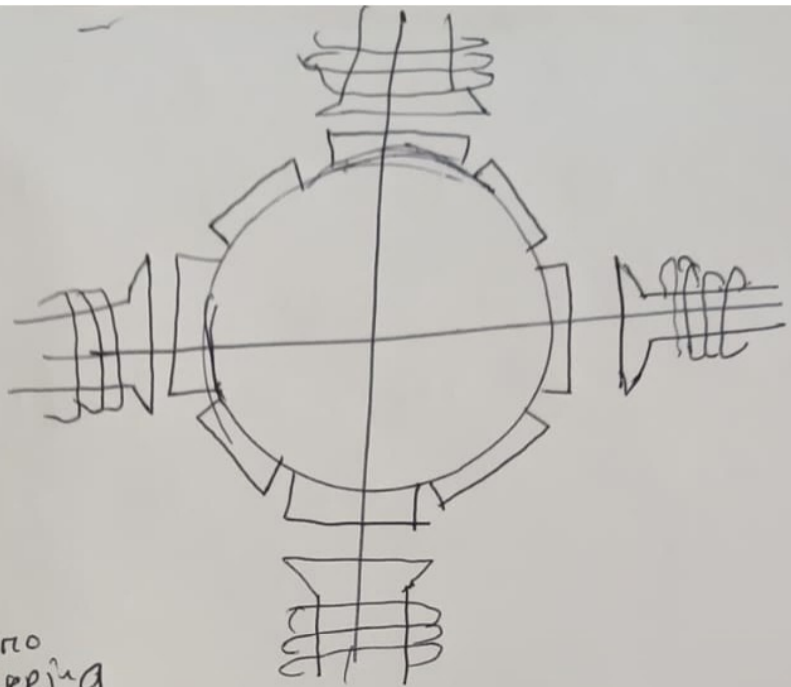

Vid-25: Servos and uses:

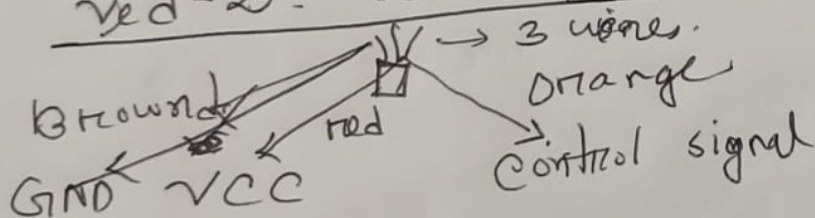

$VCC = 4.8 \sim 7.2 V.$

